

# VERIFICATION OF BOOLEAN IDENTITIES

*Rudra Pratap Singh*

## Contents

1	PROBLEM	1
2	COMPONENTS	1
3	TRUTH TABLE	2
4	ARDUINO CONNECTIONS	2
5	CODE	2

## 1 PROBLEM

(GATE CS-2008) Q.5 In the Karnaugh map shown below, X denotes a don't care term. What is the minimal form of the function represented by the Karnaugh map?

$cd \backslash ba$	00	01	11	10
00	1	1	0	1
01	X	0	0	0
11	X	0	0	0
10	1	1	0	X

Table 1

$cd \backslash ba$	00	01	11	10
00	1	1	0	1
01	X	0	0	0
11	X	0	0	0
10	1	1	0	X

Table 2

$cd \backslash ba$	00	01	11	10
00	1	1	0	1
01	X	0	0	0
11	X	0	0	0
10	1	1	0	X

One group is {0000, 0001, 1000, 1001} (Table 1) which gives  $a'd'$ .

Another group consists of {0000, 0010, 1000, 1010} (Table 2) which gives  $b'd'$ .

Hence, the correct option is **a**).

(A)  $b'd' + a'd'$

(B)  $a'b' + b'd' + a'bd'$

(C)  $b'd' + a'bd'$

(D)  $a'b' + b'd' + a'd'$

## 2 COMPONENTS

Component	Value	Quantity
Arduino	UNO	1
Bread board	-	1
Jumper wires	M-M	10
LED	-	1

### 3 TRUTH TABLE

The Truth Table for the identity is as follows:

(A)  $Y = b'd' + a'd'$

<b>a</b>	<b>b</b>	<b>d</b>	<b>Y</b>
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Table 1

### 4 ARDUINO CONNECTIONS

1) The connections taken from Arduino as Input and Output is as follows:

Input	$a$	$b$	$d$	$Y$
Arduino	3	4	5	6

Table 2

2) The input **a,b,c** here are connected to Arduino D3,D4,D5 pins.

3) The output **Y** here are connected to Arduino D6 pins.

4) The values for these inputs are connected either to GND or 5V according to the truth table.

### 5 CODE

The arduino code can be downloaded from the below link.

<https://github.com/Rudrapratap1404/Rudrapratap1404/blob/main/ide/code/src/GATE2008.cpp>